

Name _____

PHY2049C, Practice Quiz 8


A- Read all the quiz once, or twice, before beginning to write. Make sure to comprehend all questions and start with those you feel most confident.

B – Be clear and concise. There are no extra points for being verbose or writing extra.

C –Only use the white pages that I will provide. You have 60 minutes to answer the quiz.

Problem 1

The Figure shows three circuits with identical batteries, inductors, and resistors. Rank the circuits, greatest first, according to the current through the resistor labeled R (a) long after the switch is closed. (b) just after the switch is reopened a long time later, and (c) long after it is reopened.

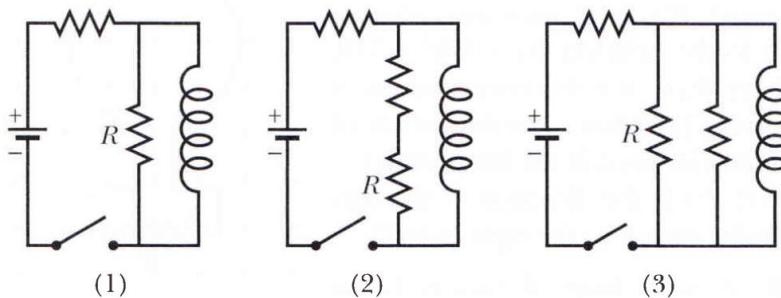


Problem 2

A square wire loop with 2.00 m sides is perpendicular to a uniform magnetic field, with half the area of the loop in the field as shown in the figure. The loop contains an ideal battery with emf $V = 20.0$ V. If the magnitude of the field varies with time according to


$$B = -0.0420 - 0.870t,$$

with B in teslas and t in seconds, what is the net emf in the circuit?

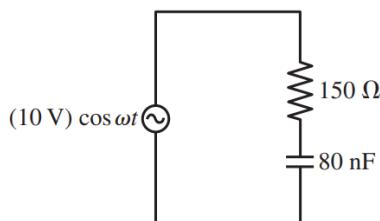


Problem 3

What are V_R and V_C if the emf frequency in the figure is 10 kHz?

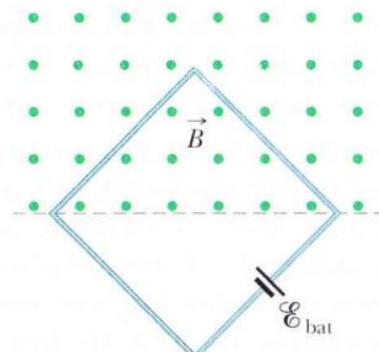

Problem 4

The figure shows an N -turn rectangular coil of length a and width b entering a region of uniform magnetic field of uniform magnitude B , directed into the page. The velocity of the coil is constant and is upward in the figure. The total resistance of the coil is R . What is the induced emf when (a) only a portion of the coil has entered the region with the field, (b) the whole coil has entered the field.

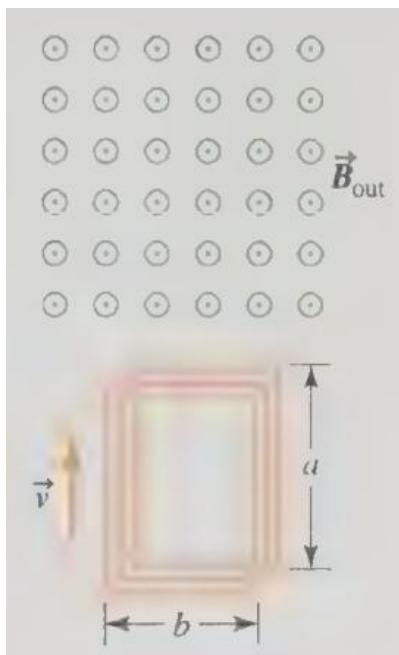

Problem 5

What is the peak voltage across the 3.0 mF capacitor?

